

Contents

1	General CPU Register	5
1.1	Diagram	5
1.2	I/O Control	5
1.3	Working	5
2	Program Counter	5
2.1	Diagram	5
2.2	PC_INC	6
2.3	PC_OUT	6
2.4	PC_LOAD	6
3	MEMORY	7
3.1	Diagram	7
3.2	Diagram	7
3.3	MEM_OUT	7
4	MEMORY ADDRESS REGISTER	7
4.1	MAR_IN	8
5	INSTRUCTION REGISTER	8
5.1	Diagram	8
5.2	INS_REG_IN	8
5.3	INS_REG_OUT	8
5.4	CTRL	9
6	INSTRUCTION DECODER	9
6.1	Diagram	9
6.2	INS_DEC_OUT	9
6.3	ALU_OUT	9
7	Arithmetic and Logic Unit(ALU)	10
7.1	ADD	10
7.2	SUB	10
7.3	SHIFT	10
8	Status Register	11
8.1	Diagram	11
8.2	I/O	11
8.3	Uses	11
9	Control Processor	12
9.1	Diagram	12
9.2	I/O	12
9.3	Working	12
9.4	Ring Counter	12
9.5	EEPROM Programming	13

10 Microinstructions and Controller Logic Design	13
10.1 NOP :	13
10.2 LDA :	13
10.3 ADD :	13
10.4 SUB :	14
10.5 LDI :	14
10.6 JMP :	14
10.7 SWAP :	15
10.8 JNZ :	15
10.9 MOVAB :	15
10.10MOVBA :	16
10.11LSHIFT :	16
10.12RSHIFT :	16
10.13OUT :	16
10.14HLT :	17
11 Instruction Set	18
11.1 NOP :	18
11.2 LDA :	18
11.3 ADD :	18
11.4 SUB :	19
11.5 LDI :	20
11.6 JMP :	20
11.7 SWAP :	21
11.8 JNZ :	21
11.9 MOVAB :	21
11.10MOVBA :	22
11.11LSHIFT :	23
11.12RSHIFT :	23
11.13OUT :	23
11.14HLT :	24
12 Sample programs	25
12.1 For Addition and Subtraction	25
12.2 For L-shift	25
12.3 For Multiplication	25

List of Figures

1	8-bit Register	5
2	Program Counter	6
3	Memory	7
4	EEPROM	7
5	Instruction Register	8
6	Instruction Decoder	9
7	Gajendra ALU	10
8	Status Register	11
9	Control Processor	12
10	Micro Instruction for NOP	13
11	Micro instruction for LDA	13
12	Micro instruction for ADD	13
13	Micro instruction for SUB	14
14	Micro instruction for LDI	14
15	Micro instruction for JMP	14
16	Micro instruction for SWAP	15
17	Micro instruction for JNZ	15
18	Micro instruction for MOVAB	15
19	Micro instruction for MOVBA	16
20	Micro instruction for LSHIFT	16
21	Micro instruction for RSHIFT	16
22	Micro instruction for OUT	17
23	Micro instruction for HLT	17
24	Instruction Set for NOP	18
25	Instruction Set for LDA	18
26	Instruction Set for ADD	19
27	Instruction Set for SUB	19
28	Instruction Set for LDI	20
29	Instruction Set for JMP	20
30	Instruction for SWAP	21
31	Instruction Set for JNZ	21
32	Instruction Set for MOVAB	22
33	Instruction Set for MOVBA	22
34	Instruction Set for LSHIFT	23
35	Instruction Set for RSHIFT	23
36	Instruction Set for OUT	24
37	Instruction Set for HLT	24

1 General CPU Register

1.1 Diagram

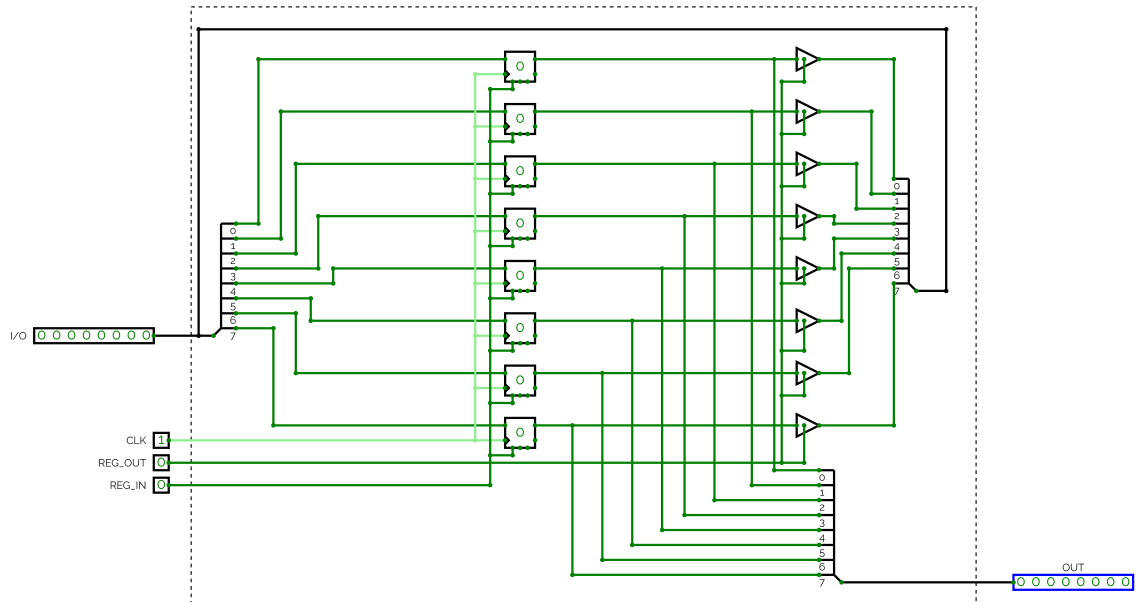


Figure 1: 8-bit Register

1.2 I/O Control

It takes 8-bit input from the common bus. Which is stored in it. The 8-bit value stored in it is given as output. REG_in and REGout are used as the control inputs for controlling the input and output.

1.3 Working

If REG_in is 1 the input is read from the common bus and when REG_out is 1 the output is written to the common bus.

2 Program Counter

2.1 Diagram

The ROM consists of both the instructions and data for the program that has to be run , The program counter points to the address of the instruction in ROM , that has to be processed

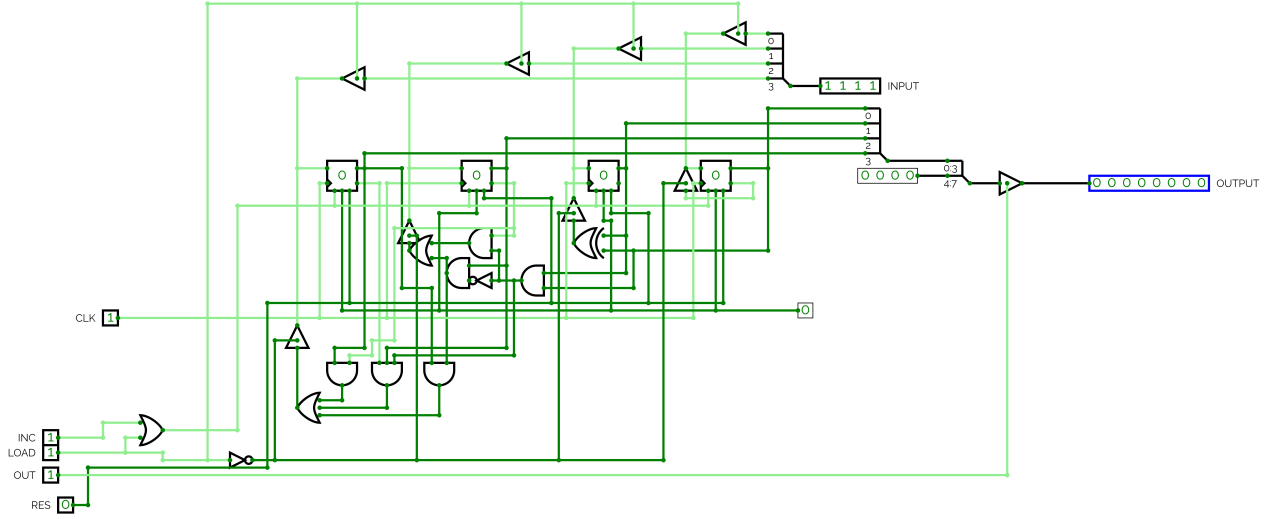


Figure 2: Program Counter

next . At the starting of the program the program counter is reset to 0000 , It then sends the address that is stored in it (i.e 0000 in this case) to the Memory Address Register , The program counter is then incremented by 1 (i.e to 0001 in this case) , After the first instruction is executed then the program counter sends the current address stored in it (i.e 0001 in this case) , this cycle keeps on repeating until the program ends.

The following are the functionalities that are present in the Program Counter.

2.2 PC_INC

If $PC_INC = 1$ then the value of the address stored in the Program Counter is incremented by 1 in each positive clock triggering .

2.3 PC_OUT

If $PC_OUT = 1$ then the Program Counter sends the address stored in it into the Least Significant Bits (0-3) of the **common bus** of the **Gajendra Processor** through **output** .

2.4 PC_LOAD

If $PC_LOAD = 1$ then the Program Counter takes the Least Significant Bits (0-3) of the **common bus** into it through the **input** and stores it as the next instruction .

3 MEMORY

3.1 Diagram

 


Figure 3: Memory

3.2 Diagram

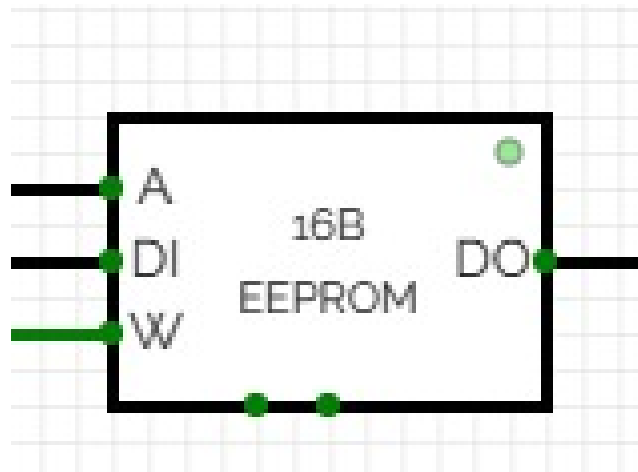


Figure 4: EEPROM

Memory is a ROM which contains both instruction and data required for a program. The following are the functionalities that are present in the Memory. We are using EEPROM here for STA instruction .

3.3 MEM_OUT

If $\text{MEM_OUT} = 1$ then the memory releases a 8-bit output into the common bus.

4 MEMORY ADDRESS REGISTER

During a computer run , the 4-bit address in the Programming Counter is latched into the MAR .Then the MAR applies this 4-bit address to the Memory where a read operation is performed. The following are the functionalities that are present in the MAR .

4.1 MAR_IN

If $MAR_IN = 1$, then the MAR takes the 4-bit address (Least Significant in common bus) from the Program Counter through common bus.

5 INSTRUCTION REGISTER

5.1 Diagram

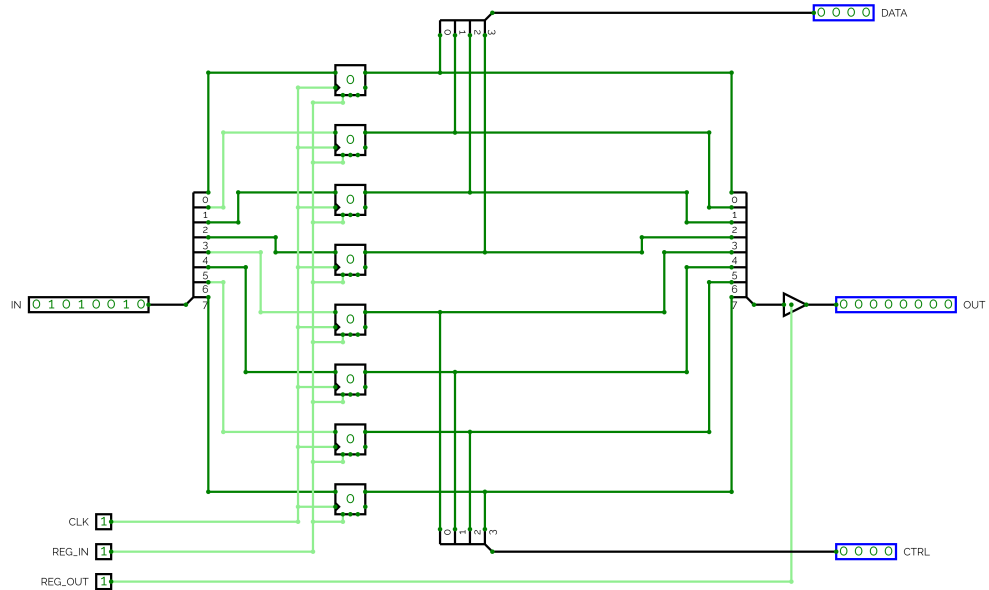


Figure 5: Instruction Register

To fetch an instruction from the memory the computer does a memory read operation . This places the contents of the addressed memory location on the common bus. The instruction register loads this content into it on the next positive clock edge .

The contents of the instruction register are split into two nibbles of 4-bits each (least 4 significant bits , most 4-significant bits) , The most 4-significant bits are sent into **Controller** and it will also send the 8-bit content into the **Instruction decoder** .

The following are the functionalities that are present in the Instruction register .

5.2 INS_REG_IN

If $INS_REG_IN = 1$, then the INS register takes the 8-bit content as input from the common bus .

5.3 INS_REG_OUT

If $INS_REG_OUT = 1$, then INS register loads its 8-bit content into Instruction decoder which further enter into the common bus .

5.4 CTRL

The Most Significant 4-bits(4-7) automatically goes to the **Controller** and **INS Decoder** as instruction from INS Register.

6 INSTRUCTION DECODER

6.1 Diagram

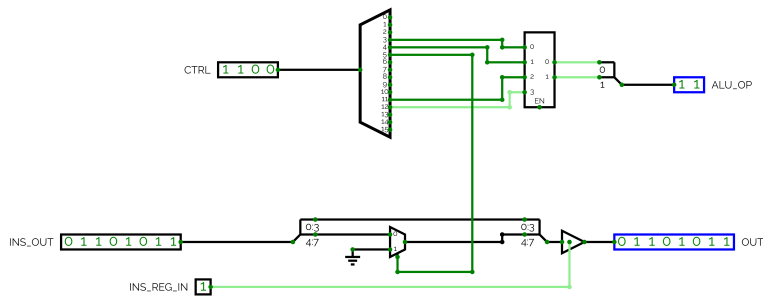


Figure 6: Instruction Decoder

It helps the ALU by giving the instruction whether to add or subtract , by using the most significant 4-bits (i.e CTRL) . It also helps us with the instruction **LDI** by making the 4 - most significant bits into 0000 , so that the remaining 4-bits gets stored in our **accumulator (i.e register A)**.

The following are the functionalities that are present in the Instruction Decoder .

6.2 INS _DEC _OUT

If $INS_DEC_OUT = 1$, then it takes the 8-bit content from OUT of INS register.

6.3 ALU_OUT

The INS_DEC generates a 2-bit input for the **ALU**.

It generates the following outputs for the corresponding instructions .

00 \implies Addition

01 \implies *Subtraction*

$$10 \implies LShift$$

$$11 \implies RShift$$

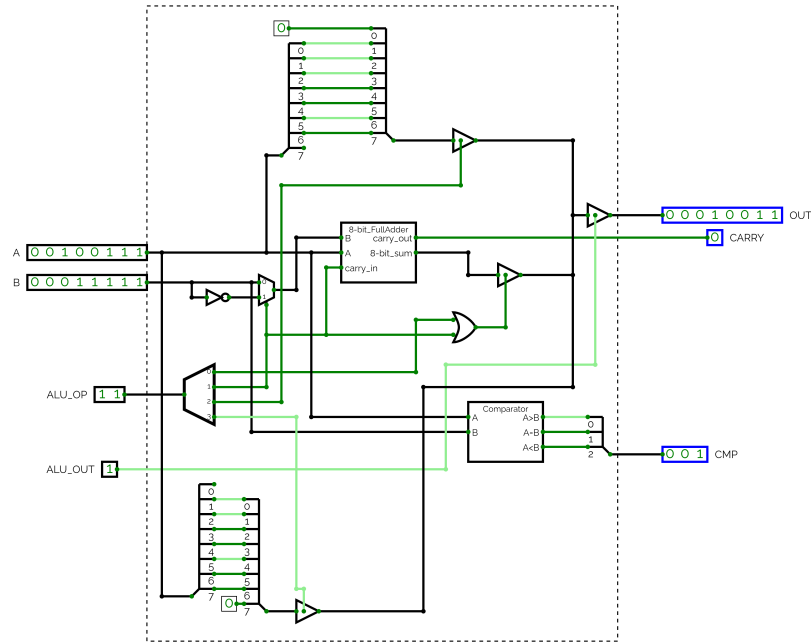


Figure 7: Gajendra ALU

7 Arithmetic and Logic Unit(ALU)

The ALU performs the arithmetic operations that are executed by the computer. The operations that are supported are Addition(ADD) , Subtraction(SUB) and SHIFT . It stores the final value in it and it also returns the final 8-bit into Accumulator or REG _A .

7.1 ADD

The ADD operation is used to add two 8-bit numbers using a 8-bit full adder which adds without carry .

7.2 SUB

The SUB operation is used to subtract two 8-bit numbers using a 8-bit full adder with an input from the INS_DEC which triggers sub operation.

7.3 SHIFT

The LSHIFT operation performs a bitwise left shift on the value in register A whereas the RSHIFT operation performs a bitwise right shift on the value in register A.

 


Figure 8: Status Register

8 Status Register

8.1 Diagram

8.2 I/O

It takes 2 inputs ALU _OUT and Carry from ALU and gives a 4-bit output in which the **the most significant bit is C**(1 if carry = 1) and the next bit gives **NC**(\overline{C}) and the next bit gives **Z**(1 if(ALU _OUT = 1) and the least significant gives **NZ** \overline{Z} .

8.3 Uses

It is used to implement JUMP and JUMP if zero conditions .

9 Control Processor

9.1 Diagram

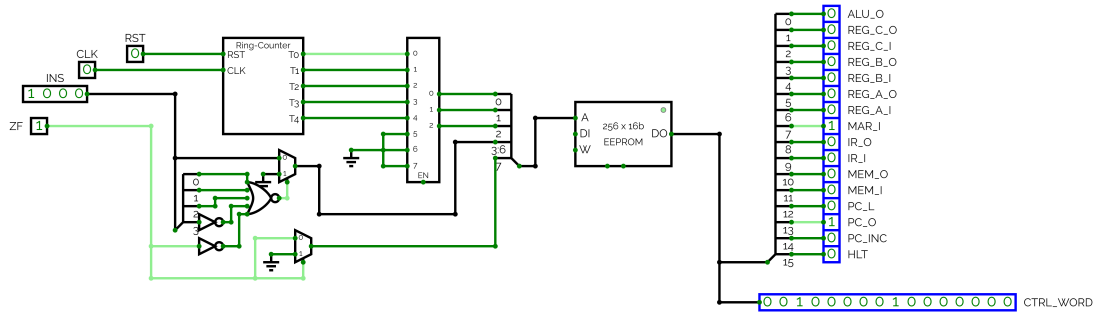


Figure 9: Control Processor

9.2 I/O

The control processor takes 4 bit instruction as input and we use a ring counter of length 5 indicating the 5 T-states. The EEPROM in the control processor takes 8-bit address in which the first bit is inherently zero and next 4 bits are the instruction and the last 3 bits are the T-state that is to be implemented. The EEPROM gives 16-bit output which is the control word which is also the output of the Control Processor.

9.3 Working

This control word controls all the other elements like REG_in, REG_out, PC_load, PC_out, PC_inc, flag, MEM_in, MEM_out, MAR_in, INS_out, INS_out, ALU_out. The control processor is the most important component of our processor as it controls all the other components. When Ins is 1000 (JNZ) and ZF = 1, this instruction changes to NOP (0000) and the MSB of address entering into EEPROM will also be 0 (i.e the ZF will enter A as 0). In this way other half of the EEPROM need not be wasted and optimized.

9.4 Ring Counter

Every instruction has some micro instructions called T-states that are to be executed in order one at a time, these control words are generated by accessing the memory locations in the EEPROM, the T-states are governed by the ring counter.

9.5 EEPROM Programming

The EEPROM is loaded in such a way that every instruction has 8 memory locations in the EEPROM for its micro instructions. The each memory locations contains the control word of that particular micro instruction.

10 Microinstructions and Controller Logic Design

10.1 NOP :

NOP :	1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	0	T2
	0	T3
	0	T4

Figure 10: Micro Instruction for NOP

10.2 LDA :

LDA :	1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<MAR_IN	T2
	1<<MEM_OUT 1<<REGA_IN	T3
	0	T4

Figure 11: Micro instruction for LDA

10.3 ADD :

ADD :	1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<MAR_IN	T2
	1<<MEM_IN 1<<REGA_OUT	T3
	0	T4

Figure 12: Micro instruction for ADD

10.4 SUB :

SUB	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<MAR_IN	T2
	1<<MEM_IN 1<<REGA_OUT	T3
	0	T4

Figure 13: Micro instruction for SUB

10.5 LDI :

LDI	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<REGA_IN	T2
	0	T3
	0	T4

Figure 14: Micro instruction for LDI

10.6 JMP :

JMP	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<PC_LOAD	T2
	0	T3
	0	T4

Figure 15: Micro instruction for JMP

10.7 SWAP :

SWAP	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<REGA_OUT 1<<REGB_IN	T2
	1<<REGC_OUT 1<<REGA_IN	T3
	1<<REGB_OUT 1<<REGC_IN	T4

Figure 16: Micro instruction for SWAP

10.8 JNZ :

JNZ	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<PC_LOAD	T2
	0	T3
	0	T4

Figure 17: Micro instruction for JNZ

10.9 MOVAB :

MOVAB	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<REGA_OUT 1<<REGB_IN	T2
	0	T3
	0	T4

Figure 18: Micro instruction for MOVAB

10.10 MOVBA :

MOVBA:1<<PC_OUT 1<<MAR_IN	T0
1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
1<<REGB_OUT 1<<REGA_IN	T2
0	T3
0	T4

Figure 19: Micro instruction for MOVBA

10.11 LSHIFT :

SHIFT:1<<PC_OUT 1<<MAR_IN	T0
1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
1<<ALU_OUT 1<<REGA_IN	T2
0	T3
0	T4

Figure 20: Micro instruction for LSHIFT

10.12 RSHIFT :

SHIFT:1<<PC_OUT 1<<MAR_IN	T0
1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
1<<ALU_OUT 1<<REGA_IN	T2
0	T3
0	T4

Figure 21: Micro instruction for RSHIFT

10.13 OUT :

OUT	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<REGA_OUT 1<<REGC_IN	T2
	0	T3
	0	T4

Figure 22: Micro instruction for OUT

10.14 HLT :

HLT	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<HLT	T2
	0	T3
	0	T4

Figure 23: Micro instruction for HLT

11 Instruction Set

11.1 NOP :

Description

Loads the Instruction Register and increments the Program Counter.

Operation:

(i) (i)None

Syntax:

(i) NOP X

Operands:

None

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

0000	XXXX
------	------

Figure 24: Instruction Set for NOP

11.2 LDA :

Description

Loads the value stored in the address into the accumulator.

Operation:

(i) (i) $R_A \leftarrow *X$

Syntax:

(i) LDA X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

0001	XXXX
------	------

Figure 25: Instruction Set for LDA

11.3 ADD :

Description

Stores the value in the given address in register B and adds that value to the accumulator.

Operation:

- (i) $R_B \leftarrow *X$
 (ii) $R_A \leftarrow R_A + R_B$

Syntax:

- (i) ADD X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

0011	xxxx
------	------

Figure 26: Instruction Set for ADD

11.4 SUB :

Description

Stores the value in the given address in register B and subtracts it from the value in the accumulator.

Operation:

- (i) $R_B \leftarrow *X$
 (ii) $R_A \leftarrow R_A - R_B$

Syntax:

- (i) SUB X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

0100	xxxx
------	------

Figure 27: Instruction Set for SUB

11.5 LDI :

Description

Loads the given value into the accumulator.

Operation:

(i) $(i)R_A \leftarrow X$

Syntax:

(i) LDI X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

0101	xxxx
------	------

Figure 28: Instruction Set for LDI

11.6 JMP :

Description

Jumps to the given address unconditionally.

Operation:

(i) $(i)PC \leftarrow k$

Syntax:

(i) JMP k

Operands:

$0 \leq k \leq 15$

Program Counter:

$PC \leftarrow k$

8-bit op-code:

0110	kkkk
------	------

Figure 29: Instruction Set for JMP

11.7 SWAP :

Description

Swaps the values in registers A and C using the register B.

Operation:

- (i) $R_B \leftarrow R_A$
- (ii) $R_A \leftarrow R_C$
- (iii) $R_C \leftarrow R_B$

Syntax:

- (i) SWAP X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

0111	xxxx
------	------

Figure 30: Instruction for SWAP

11.8 JNZ :

Description

Jumps to the given address only if the NZ flag is 0 else it acts as NOP.

Operation:

- (i) $PC \leftarrow k / PC \leftarrow PC + 1$

Syntax:

- (i) JNZ X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow k / PC \leftarrow PC + 1$$

8-bit op-code:

1000	xxxx
------	------

Figure 31: Instruction Set for JNZ

11.9 MOVAB :

Description

Copies the value in register B to register A and retains the value in register B.

Operation:

(i) $(i)R_A \leftarrow R_B$

Syntax:

(i) MOVAB X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

1001	xxxx
------	------

Figure 32: Instruction Set for MOVAB

11.10 MOVBA :

Description

Copies the value in register B to register A and retains the value in register B.

Operation:

(i) $(i)R_B \leftarrow R_A$

Syntax:

(i) MOVBA X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

1010	xxxx
------	------

Figure 33: Instruction Set for MOVBA

11.11 LSHIFT :

Description

Bitwise shifts the value in register A by one bit to the left, discarding the leftmost bit and introducing a zero at the rightmost bit.

Operation:

(i) $R_A \ll 1$

Syntax:

(i) LSHIFT X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

1011	xxxx
------	------

Figure 34: Instruction Set for LSHIFT

11.12 RSHIFT :

Description

Bitwise shifts the value in register A by one bit to the right, discarding the rightmost bit and introducing a zero at the leftmost bit.

Operation:

(i) $R_A \gg 1$

Syntax:

(i) RSHIFT X

Operands:

$0 \leq x \leq 15$

Program Counter:

$PC \leftarrow PC + 1$

8-bit op-code:

1100	xxxx
------	------

Figure 35: Instruction Set for RSHIFT

11.13 OUT :

Description

Copies the value in Register A to Register C and the value is displayed on the screen.

Operation:

- (i) $(i)R_A \leftarrow X$

Syntax:

- (i) OUT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

1101	xxxx
------	------

Figure 36: Instruction Set for OUT

11.14 HLT :

Description

Terminates the program i.e, no further instruction is executed unless the system is restarted.

Operation:

- (i) $(i)R_A \leftarrow X$

Syntax:

- (i) HLT X

Operands:

$$0 \leq x \leq 15$$

Program Counter:

$$PC \leftarrow PC + 1$$

8-bit op-code:

1110	xxxx
------	------

Figure 37: Instruction Set for HLT

12 Sample programs

12.1 For Addition and Subtraction

Load for EEPROM for the Addition and Subtraction Program :
(0x1c,0x3f,0x4d,0xd0,0xe0,0,0,0,0,0,0,0,0x03,0x02,0x00,0x05)

```
LOAD c
ADD f
SUB d
OUT
HALT
```

0xd : 2
0xc : 3
0xf : 5

12.2 For L-shift

Load for EEPROM for the L-shift Program :
(0x56,0xb0,0xd0,0xe0,0,0,0,0,0,0,0,0,0,0,0,0)

```
LDI 6
LSHIFT
OUT
HALT
```

12.3 For Multiplication

This example is for 3*5 .(CUSTOM values can be given in the mentioned places). Load for EEPROM for the multiplication of 3 and 5 :

(0x1a,0x3c,0x2e,0x1d,0x4b,0x2d,0x1e,0x81,0xd0,0xe0,0x00,0x01,0x03,0x05,0x00,0x00)
0x03,0x05 (i.e c, d can be changed)

```
LDA a
ADD c
STA e
LDA d
SUB b
STA d
LDA e
JNZ 1 (To 2nd step(i.e ADD c))
OUT
HALT
```

0xA : 0
0xb : 1
0xc : 3
0xd : updated value of the cycle i= 5 .
0xe : value of final value after n cycles in loop (i.e 3*n) is stored .